 


SEQUENTIAL CIRCUITS

NCTU-EE IC LAB FALL-2021



Lecturer: Yi-Ching Wang

Outline

- ✓ **Section 1 Sequential Circuits**
- ✓ **Section 2 Finite State Machine**
- ✓ **Section 3 Timing**
- ✓ **Section 4 Synthesis and Design Compiler**



Outline

✓ Section 1 Sequential Circuits

✓ Introduction

✓ Syntax

✓ Reset


✓ Coding Style

✓ Generate & For Loop




Motivation

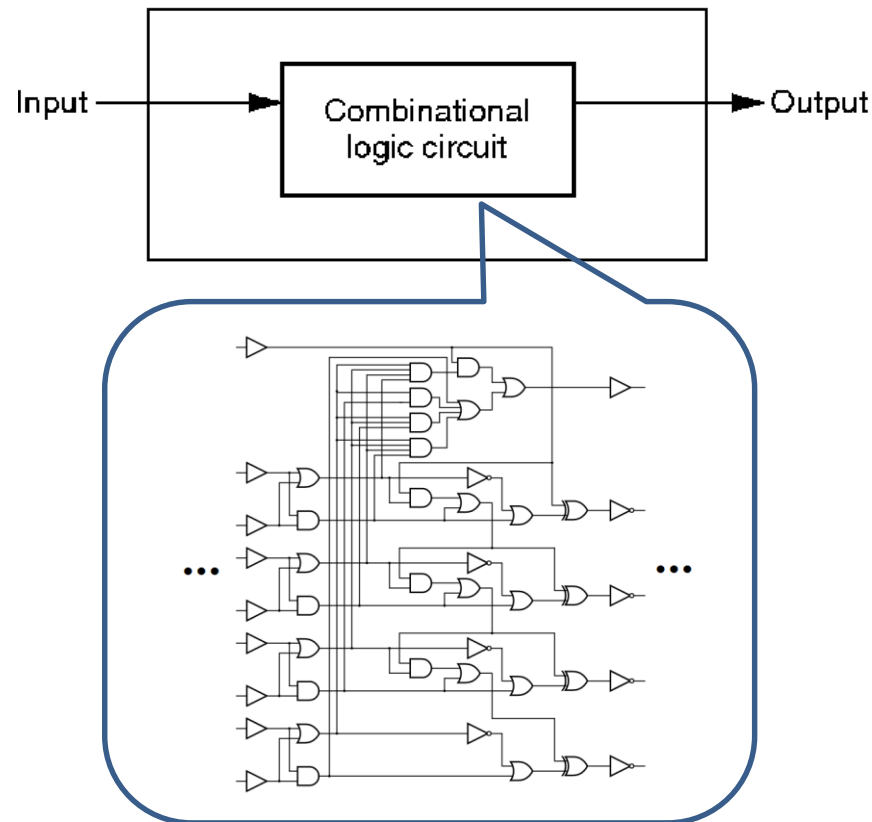- ✓ **Progress so far : Combinational circuit**
 - Output is only a function of the **current** input values



Motivation

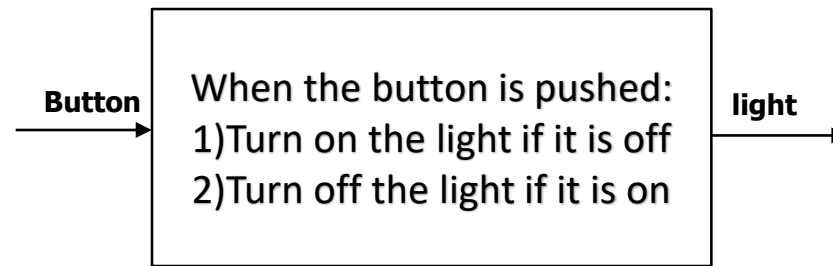- ✓ What if you were given the following design specification:



- ✓ What makes this circuit so different from we've discussed before?

“State”




What is Sequential Circuit ?

✓ Sequential circuit

- Output depends not only on the current input values, but also on **preceding** input values
- It remembers sort of the past history of the system


✓ How?

- Registers(Flip-Flops)

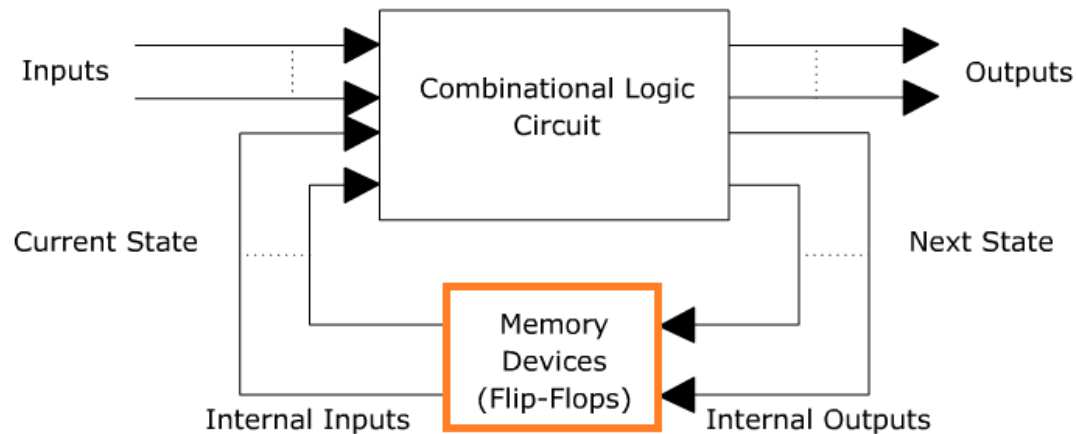


Flip-Flop Operation

✓ Latch: level sensitive

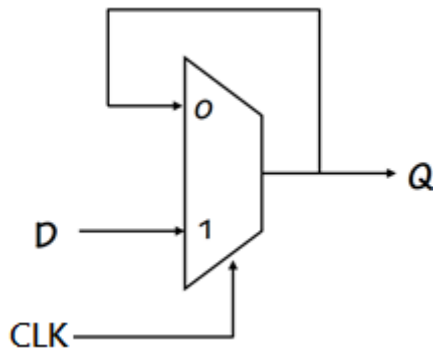


CLK	D	Q	Q'	
0	--	0	0	} Q stable
0	--	1	1	
1	0	--	0	} Q follows D
1	1	--	1	

CLK=1 : Q follows D
CLK=0 : Q holds

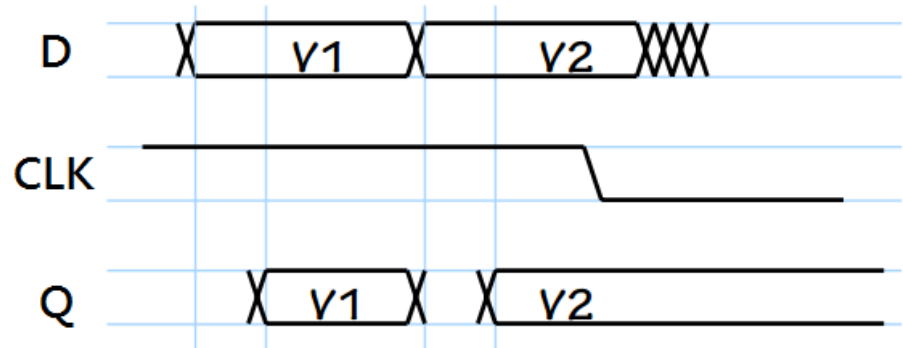


Flip-Flop Operation

✓ D flip-flop: edge triggered

 

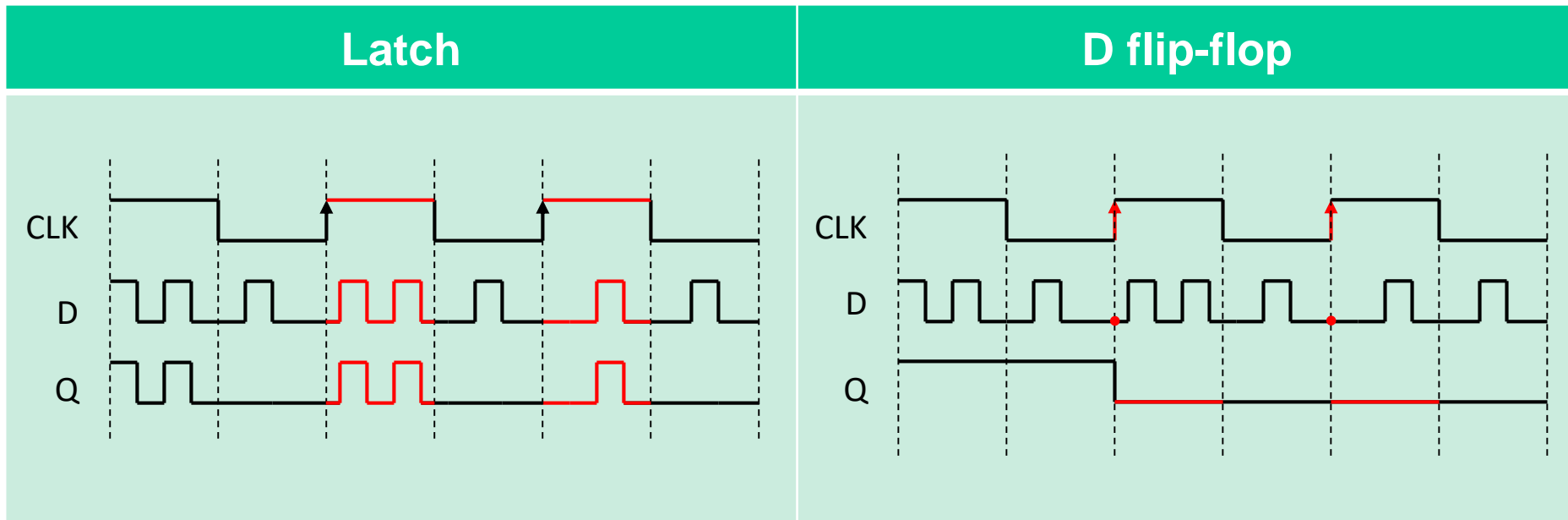✓ Positive latch v.s. positive D flip-flop





Coding Styles (1/3)

✓ Example

```
always @(*)  
begin  
    if(sel == 1) f = a;  
    else f = b;  
end
```
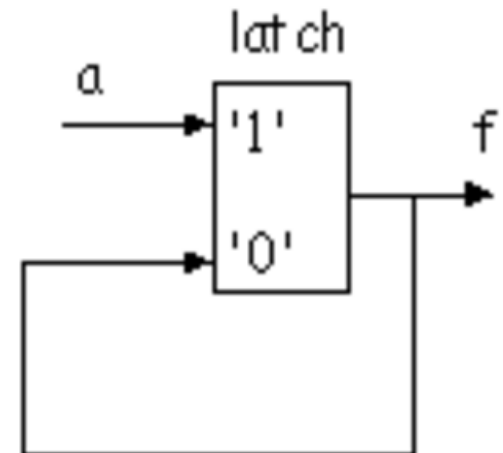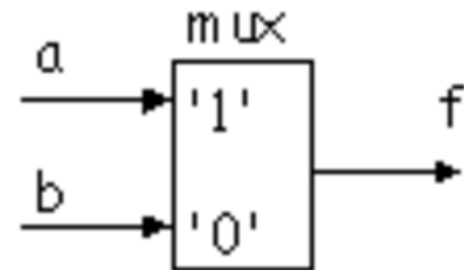
```
always @(*)  
begin  
    if(sel == 1) f = a;  
end
```



Coding Styles (2/3)

✓ Avoid latches in combinational circuit

- Avoid incomplete if-then-else
- Avoid incomplete case statements

X

```
if(!rst_n) out = 0;  
else if(m==3'd0) out = m0_out;  
else if(m==3'd1) out = m1_out;
```

X

```
case(mode)  
  3'd0: out = m0_out;  
  3'd1: out = m1_out;  
endcase
```

O

```
if(!rst_n) out = 0;  
else if(m==3'd0) out = m0_out;  
else if(m==3'd1) out = m1_out;  
else out = default_out;
```

O

```
case(mode)  
  3'd0: out = m0_out;  
  3'd1: out = m1_out;  
  default:  
    out = default_out;  
endcase
```



Coding Styles (3/3)

✓ Avoid combinational feedbacks

- Lead to unpredictable oscillated output
- NOT allowed

X

```
assign a=a+1;
```

X

```
assign out_value=out;
always @(*) begin
case(mode)
    3'd0: out = m0_out;
    3'd1: out = m1_out;
    default:
        out = out_value;
endcase
end
```

X

```
always @(*) begin
    a = a+1;
end
```

X


```
always @(*) begin
    if(in_a) a = c;
    else a = a;
end
```



Flip-Flop Data Type

✓ Flip-flop: data storage element with 4 states (0,1, X, Z)

 - **0**: logic low
- **1**: logic high
- **X**: unknown, may be a 0,1, Z, or in transition
- **Z**: high impedance, floating state



✓ Operations on the 4 states

- Example: AND, OR, NOT gate

AND	0	1	X	Z
0	0	0	0	0
1	0	1	X	X
X	0	X	X	X
Z	0	X	X	X


OR	0	1	X	Z
0	0	1	X	X
1	1	1	1	1
X	X	1	X	X
Z	X	1	X	X

NOT	output
0	1
1	0
X	X
Z	X



Concept of Sequential Circuit


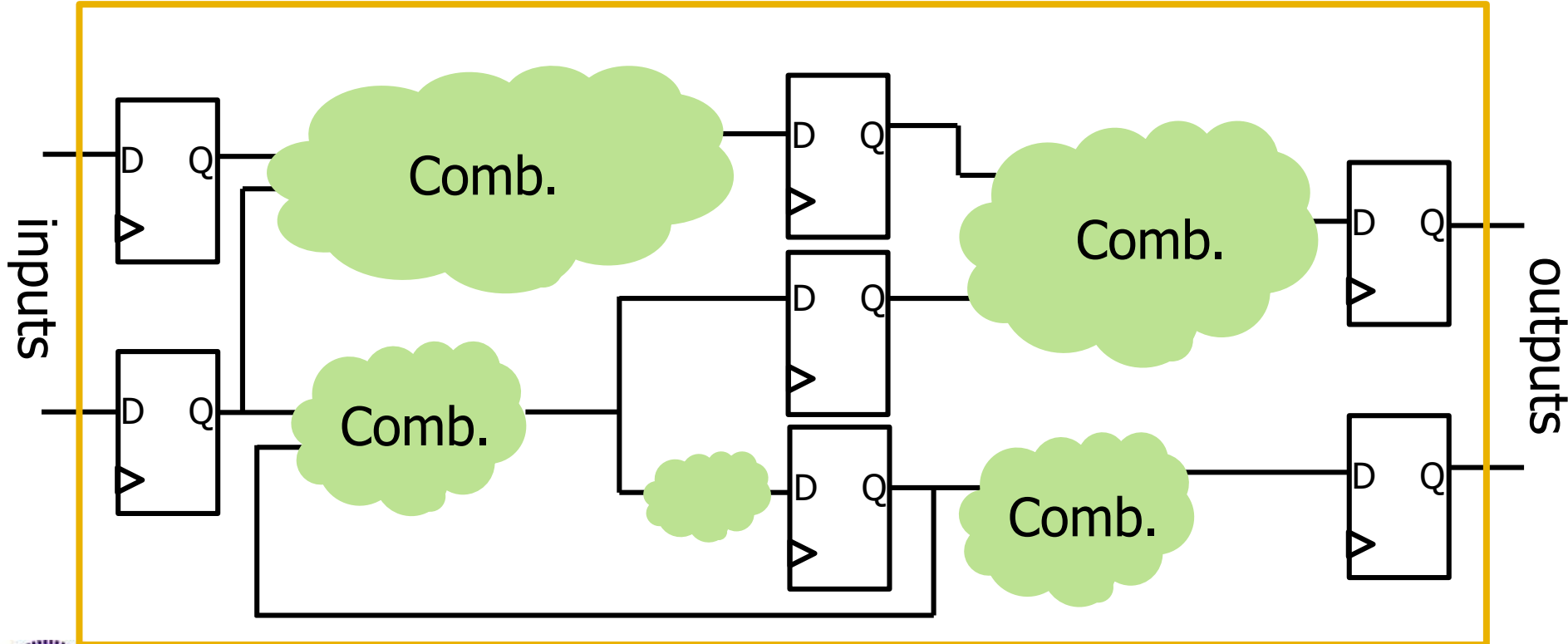
- ✓ Most computations are done by combinational circuit
 - ✓ Sequential elements are used for storage
- top design



Combinational v.s. Sequential



Combinational
  
```
always@(*)  
begin  
    if(sel) out = a;  
    else    out = b;  
end
```



Sequential
  
```
always@(posedge clk)  
begin  
    if(sel) out <= a;  
    else    out <= b;  
end
```



Outline

✓ Section 1 Sequential Circuits

✓ Introduction

✓ Syntax

✓ Reset

✓ Coding Style

✓ Generate & For Loop




Assignment in Sequential Circuit

✓ Non-blocking assignment

- Evaluations and assignments are executed **at the same time without regard to orders or dependence upon each other**
- Syntax : **<variable> <= <expression>;**

✓ Example
 
```
always @(posedge clk)
begin
    q1 <= in;
    q2 <= q1;
    out <= q2;
end
```




Assignment in Sequential Circuit

✓ Blocking assignment

- Evaluations and assignments are **immediate** and **in order**
- Syntax : **<variable> = <expression>;**

✓ Example
 
```
always @(posedge clk)
begin
    q1 = in;
    q2 = q1;
    out = q2;
end
```



Coding Styles

- ✓ Sequential blocks should only use “<=” assignments

```
always @(posedge clk) begin
    out <= out+1;
end
```

- ✓ Combinational blocks should only use “=” assignments

```
always @(*) begin
    if(sel) out = a;
    else    out = b;
end
```



Outline

✓ Section 1 Sequential Circuits

✓ Introduction

✓ Syntax

✓ **Reset**

✓ Coding Style

✓ Generate & For Loop




Synchronous Reset (1/2)

✓ Register with synchronous reset

- Syntax: `always@(posedge clk)`
 
```
always @(posedge clk) begin
    if (reset) c <= 0;
    else c <= a+1;
end
```




✓ Advantages

- Glitch filtering from reset combinational logic



✓ Disadvantages

 - Can't be reset without clock signal
- May need a pulse stretcher
 - Guarantee a reset pulse wide enough
- Larger area
- Increasing critical path



Synchronous Reset (2/2)

✓ Advantage: glitch filtering

 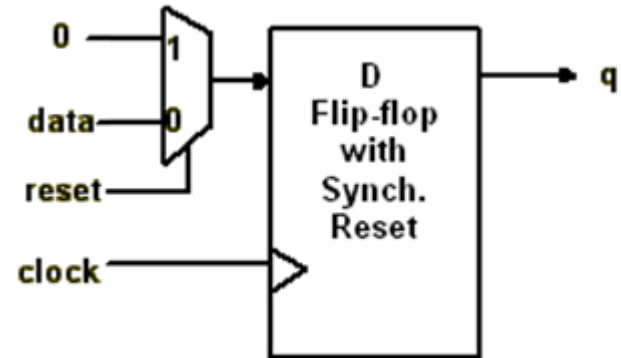


Asynchronous Reset

✓ Register with asynchronous reset

- Syntax: **always @(posedge clk or posedge reset)**
 
```
always @(posedge clk or posedge reset)
begin
    if (reset) c <= 0;
    else c <= a+1;
end
```




✓ Advantages

- Reset is independent of clock signal
- Reset is immediate
- Less area

✓ Disadvantages

 - Noisy reset line could cause unwanted reset
- Metastability




Coding Styles

- ✓ Reset all signals to avoid unknown propagation

X
 
```
always @(posedge clk) begin
    // if(!rst_n) week <= 0;
    week <= week+1;
end
always @(posedge clk) begin
    if(!rst_n) day <= 0;
    else day <= week * 7;
end
```



- ✓ Avoid conditional resets

X

```
always @(posedge clk or posedge reset or posedge a) begin
    if (reset || a) q <= 0;
    else ...
    ...
end
```



Outline

✓ **Section 1 Sequential Circuits**

✓ Introduction

✓ Syntax

✓ Reset

✓ **Coding Style**

✓ Non-synthesizable code



Coding Styles (1/2)

✓ **Naming should be readable**

✓ **Synthesizable codes**

- assign, always block, called sub-modules, if-then-else, cases, parameters, operators

✓ **Data has to be described in one always block**

- Multiple source drive is not valid

X

```
always @(posedge clk) begin
    out <= out+1;
end
always @(posedge clk) begin
    out <= a;
end
```

✓ **Always block can't exist both blocking and non-blocking assignment**

X

```
always @(posedge clk) begin
    if(reset) out = 0;
    else out <= out+in;
end
```



Coding Styles (2/2)

✓ Do not put many variables in one `always` block

- Except shift registers or registers with similar properties

bad

```
always @(posedge CLK) begin
    q2 <= in;
    if(sel==0) out <= q2;
    else if(sel==1) out <= q3;
    else out <= out;
end
```

suggested

```
always @(posedge CLK) begin
    q2 <= in;
end
always @(posedge CLK) begin
    if(sel==0) out <= q2;
    else if(sel==1) out <= q3;
    else out <= out;
end
```

✓ Use FSM (Finite State Machine)



Outline

✓ Section 1 Sequential Circuits

✓ Introduction

✓ Syntax

✓ Reset

✓ Coding Style

✓ **Generate & For loop**



Generate

SystemVerilog

3.1a	{	assertions	mailboxes	from C / C++		
		test program blocks	semaphores	classes	dynamic arrays	
	{	clocking domains	constrained random values	inheritance	associative arrays	
		process control	direct C function calls	strings	references	
3.0	{	interfaces	packages	int	globals	break
		nested hierarchy	2-state modeling	shortint	enum	continue
	{	unrestricted ports	packed arrays	longint	typedef	return
		automatic port connect	array assignments	byte	structures	do-while
	{	enhanced literals	queues	shortreal	unions	++ -- += -= *= /=
		time values and units	unique/priority case/if	void	casting	>>= <<= >>>= <<<=
	{	specialized procedures	compilation unit space	alias	const	&= = ^= %=

Verilog-2001

ANSI C style ports
generate
 localparam
 constant functions

standard file I/O
 \$value\$plusargs
 `ifndef `elsif `line
 @*

(* attributes *)
 configurations
 memory part selects
 variable part select

multi dimensional arrays
 signed types
 automatic
 ** (power operator)

Verilog-1995

modules
 parameters
 function/tasks
 always @
 assign
 \$finish \$fopen \$fclose
 \$display \$write
 \$monitor
 `define `ifdef `else
 `include `timescale

initial
 disable
 events
 wait # @
 fork-join
 wire reg
 integer real
 time
 packed arrays
 2D memory

begin-end
 while
 for forever
 if-else
 repeat
 + = * /
 %
 >> <<

For Loop

- For loop in Verilog
 - Duplicate same function
 - Very useful for doing reset and iterated operation
 - Unrolling

```
reg [3:0] temp;  
integer i;  
always @(posedge clk) begin  
  for (i = 0; i < 3 ; i = i + 1) begin: for_name  
    temp[i] <= 1'b0;  
  end  
end
```

=

```
always @(posedge clk) begin  
  temp[0] <= 1'b0;  
  temp[1] <= 1'b0;  
  temp[2] <= 1'b0;  
end
```

Generate

- How to use for loop with generate?
 - For loop in generate : four always blocks
 - Regular for loop : one always block

```
reg [3:0] temp;  
genvar i;  
generate  
for (i = 0; i < 4 ; i = i + 1) begin: for_name  
    always @(posedge clk) begin  
        temp[i] <= 1'b0;  
    end  
end  
endgenerate
```

Generate block


```
reg [3:0] temp;  
integer i;  
always @(posedge clk) begin  
    for (i = 0; i < 4 ; i = i + 1) begin:  
        temp[i] <= 1'b0;  
    end  
end
```

Regular for loop

Generate

```
reg [3:0] temp;  
  
genvar i;  
generate  
for (i=0 ; i <4; i = i+1)begin loop_1  
    always@(*)begin  
        temp[i] = operand1[i] & operand2[i];  
    end  
end  
endgenerate
```

always block in for loop with
genvar

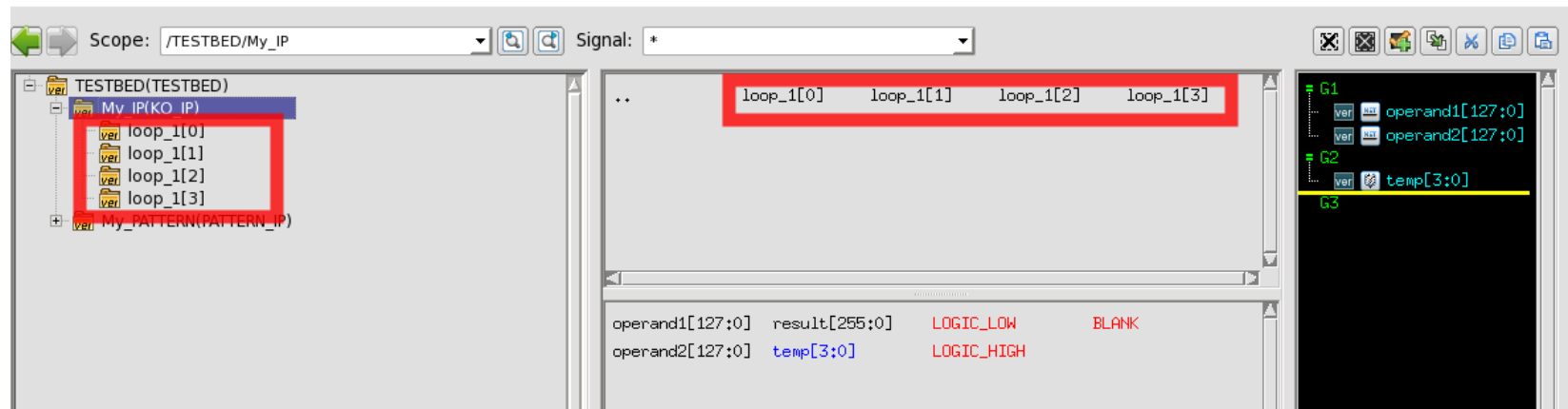

4 always block
instance

Outline


- ✓ Section 1 Sequential Circuits
- ✓ **Section 2 Finite State Machine**
- ✓ Section 3 Timing
- ✓ Section 4 Synthesis and Design Compiler



Finite State Machine

✓ Example: Vending machine

Coke \$25
Pepsi \$25
Sprite \$25

 


Finite State Machine

✓ Finite state machine

- Powerful model for describing a sequential circuit
- Divide a sequential circuit operation into finite number of states.
- A state machine controller can output results depending on the input signal, control signal and states.
- As different input or control signal changes, the state machine will take a proper state transition.

✓ State diagram

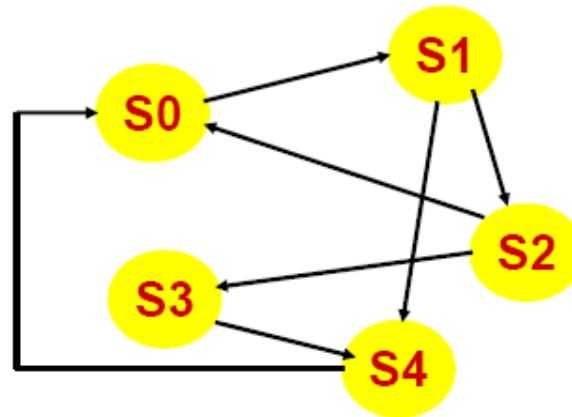

Mealy and Moore Machines


✓ Mealy machine

- The outputs depend on the current state and inputs


✓ Moore machine

- The outputs depend on the current state only

Mealy machine

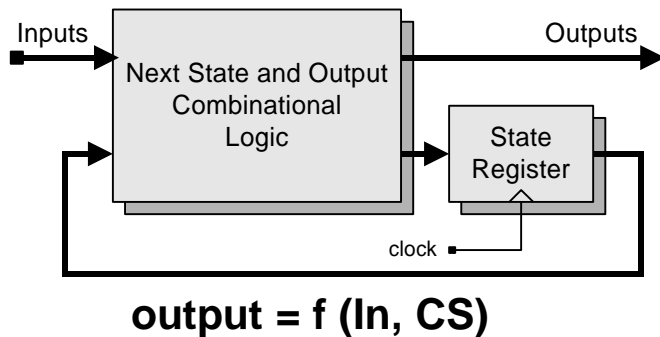

Moore machine

 

FSM Coding Style

✓ Separate current state, next state and output logic

Current State

```
always @(posedge clk or negedge rst_n) begin
    if (!rst_n) current_state <= IDLE;
    else current_state <= next_state;
end
```

Use parameters for readability

Next State

```
always @(*) begin
    if(!rst_n) next_state=IDLE;
    else begin
        case(current_state)
            STATE_1: begin
                if (in==in_1) next_state=STATE_2;
                else next_state=current_state;
            end
            STATE_2: .....
            ....
            default: next_state=current_state;
        endcase
    end
end
```

If it's not full case and without default case, latch would be incurred!


```
parameter IDLE      = 2'd0;
parameter STATE_1   = 2'd1;
parameter STATE_2   = 2'd2;
parameter STATE_3   = 2'd3;
```

Output Logic

```
always@(posedge clk or negedge rst_n) begin
    if (!rst_n) out <= 0;
    else if (current_state==STATE_3) out <= output_value;
    else out <= out;
end
```

Why FSM?

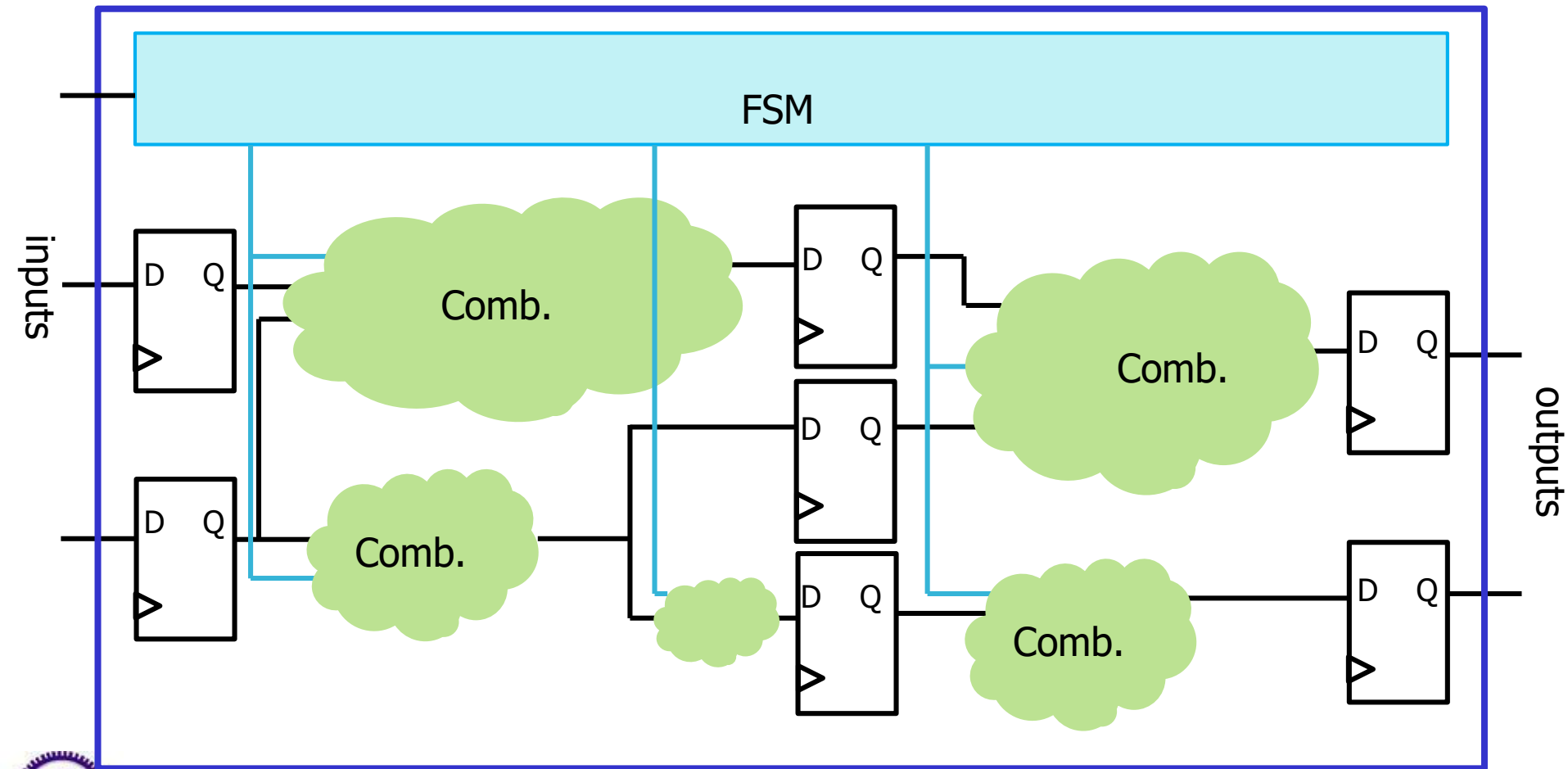- ✓ FSM can be referred to as the controller and status of the whole module



Outline


- ✓ Section 1 Sequential Circuits
- ✓ Section 2 Finite State Machine
- ✓ **Section 3 Timing**
- ✓ Section 4 Synthesis and Design Compiler



Timing Check (1/3)


✓ Setup time check

 - The `$setup` system task determines whether a data signal remains stable for a minimum specified time before a transition in an enabling, such as a clock event.




✓ Hold time check

 - The `$hold` system task determines whether a data signal remains stable for a minimum specified time after a transition in an enabling signal, such as a clock event.



Timing Check (2/3)

✓ Metastability

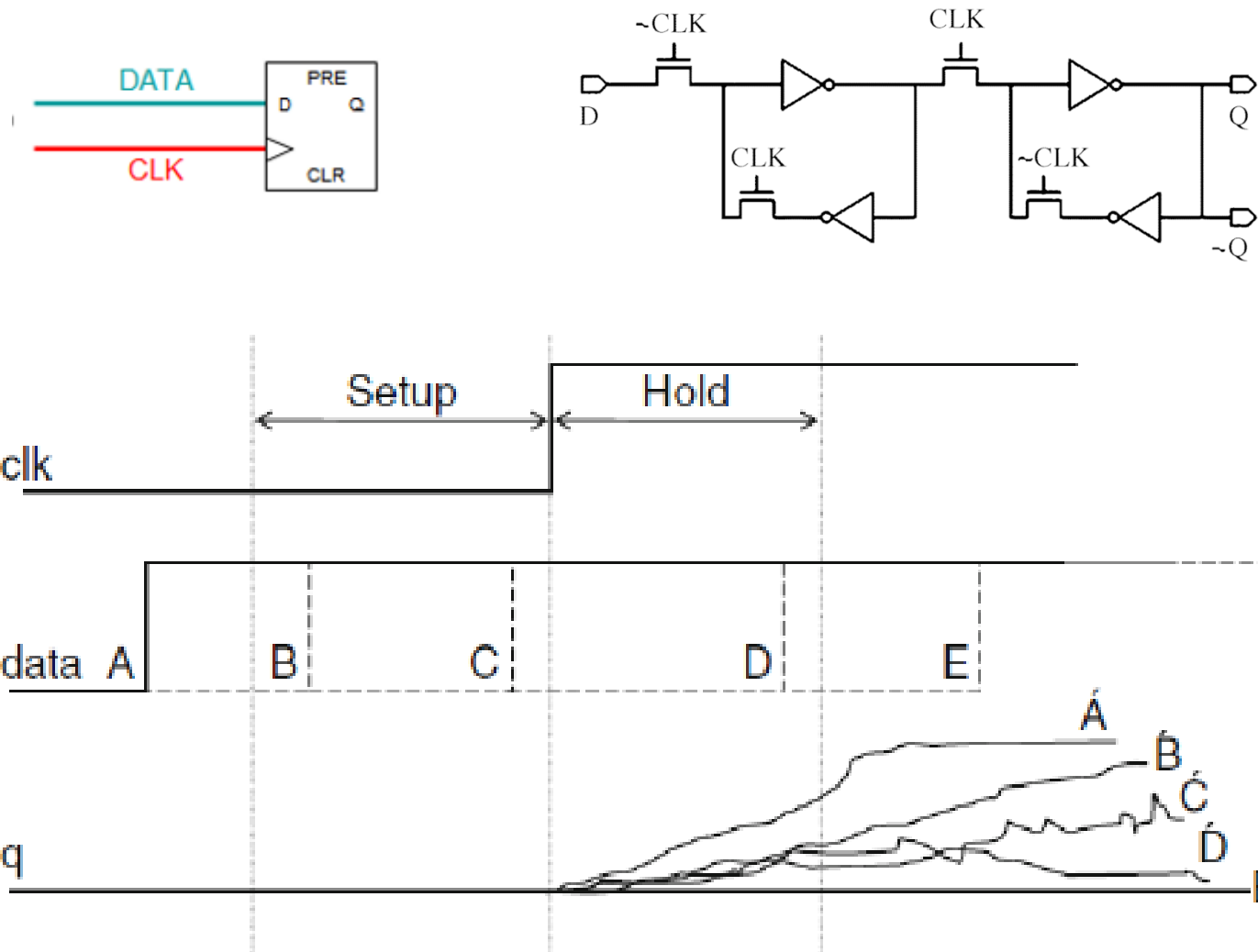

Timing Check (3/3)

✓ Timing report: setup time

clock CLK_1 (rise edge)	2.00	2.00
clock network delay (ideal)	2.00	4.00
clock uncertainty	-0.50	3.50
IN_A_reg[0]/CK (EDFFXL)	0.00	3.50 r
library setup time	-0.42	3.08
data required time		3.08

data required time		3.08
data arrival time		-3.08

slack (MET)		0.00

✓ Timing report: hold time

Slacks should be **MET**!
(non-negative)

clock CLK_2 (rise edge)	0.00	0.00
clock network delay (ideal)	4.00	4.00
clock uncertainty	1.00	5.00
IN_B_reg[20]/CK (EDFFXL)	0.00	5.00 r
library hold time	-0.19	4.81
data required time		4.81

data required time		4.81
data arrival time		-4.82

slack (MET)		0.01




Outline

- ✓ Section 1 Sequential Circuits
- ✓ Section 2 Finite State Machine
- ✓ Section 3 Timing
- ✓ **Section 4 Synthesis and Design Compiler**



Recall: Design Flow

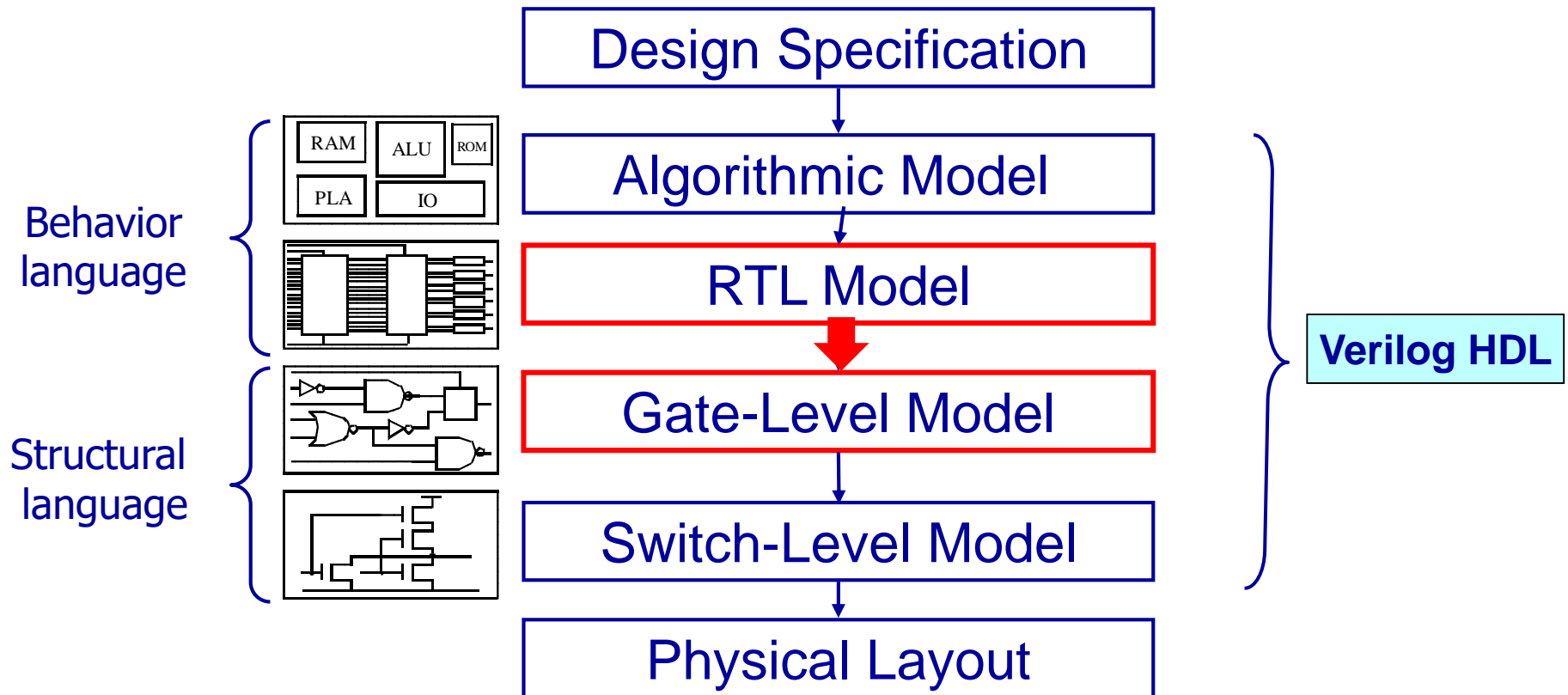

Logic Synthesis


✓ Logic synthesis

- A process by which behavioral model of a circuit is turned into an implementation in terms of logic gates
- Synthesis = **Translation+Mapping+Optimization**


```
assign avg=sum/total;  
always_ff @(posedge clk)  
begin  
    sum=sum+score*weight;  
end
```

HDL Source


Translate

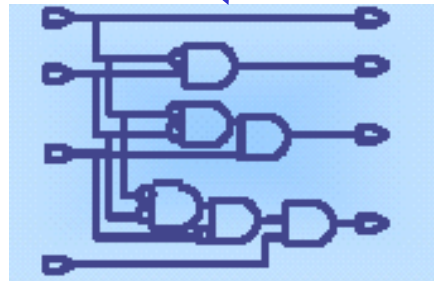

Map+Optimize

 

Target Technology

 

Design Compiler

✓ Design compiler

- A tool by Synopsys, Inc. that synthesizes your HDL designs (**Verilog**) into optimized technology-dependent, **gate-level** designs.
- It can optimize both combinational and sequential designs for speed, area, and power.

